

INSTRUMENTATION (II/II)

Course Code: ENEX - 252

(Module#2)

Dhawa Sang Dong, MSc Eng.
(Sr. Lecturer)

KATHMANDU ENGINEERING COLLEGE
Kalimati, Kathmandu

May 2025



CHAPTER#2

THEORY OF MEASUREMENT

✓ Class Outline


- 1 Introduction
- 2 Static and Dynamic Performance
- 3 Error in Measurement
- 4 Measurement of Resistance

Introduction

Theory of measurement

- The theory of measurement refers to the scientific principles and methodologies used to obtain quantitative information about physical variables using instruments.
- It is a crucial part of electrical, electronics, and mechanical engineering making measured value less erroneous.
- making error less measurement requires knowledge of characteristics and operations of instrument, basic laws to handle instrument, and cause of error.
- Therefore, study of characteristics of instruments includes
 - ✓ Error and its analysis,
 - ✓ Statistical analysis and
 - ✓ Error minimization

Static and Dynamic Performance

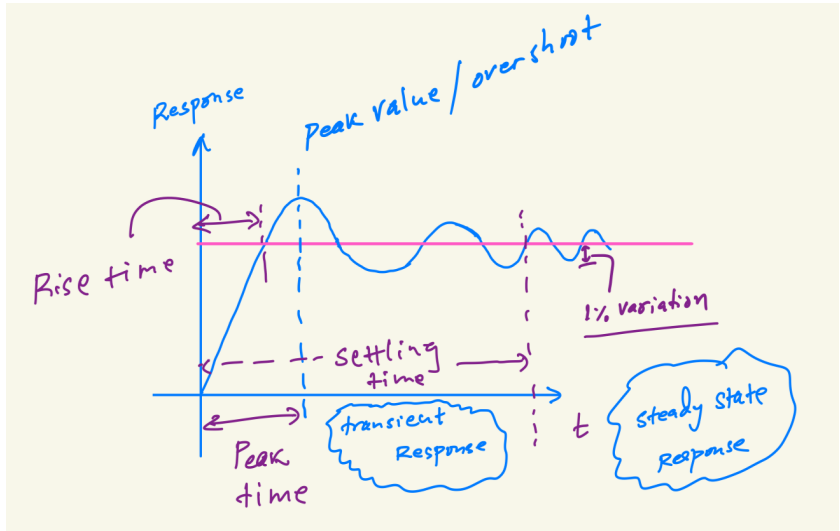

Statistical Performance Parameters

Static Characteristics

- Statistical parameters are studied during the **steady-state** of a system, not the transient phase.
- The system output is stable, so variations are due to **measurement noise, repeatability, or bias** — ideal for assessing accuracy and precision.
 - ① Accuracy
 - ② Precision or Repeatability
 - ③ Resolution
 - ④ Sensitivity
 - ⑤ Linearity

Statistical Performance Parameters

① Accuracy: | Static Characteristics

- Closeness of a measurement to the true or accepted value.

② Precision or repeatability: | Static Characteristics

- it is measure of consistency, how consistently a measurement system gives the same output for the same input under unchanged conditions.


③ Resolution: | Static Characteristics

- maximum change in input for which there is no output changed
- the minimum change in input for which there is detectable changes occur in output.

Statistical Performance Parameters

④ Sensitivity: | Static Characteristics

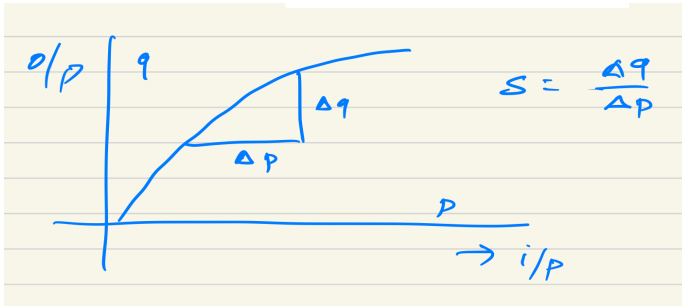- ratio of change in output to a change in input; it measures how responsive the system is.
- when the curve is linear than sensitivity is constant.



Dynamic Performance Parameters

Dynamic Characteristics

- it describes how the system behaves when the measured quantity (input) changes with time.
- they are important when the system is subjected to time-varying signals and response is not instantaneous.
 - ① Response time,
 - ② Time Constant
 - ③ Frequency Response
 - ④ bandwidth
 - ⑤ Rise time
 - ⑥ Delay time

Dynamic Performance Parameters

① Response Time: | Dynamic Characteristics

- In measurement systems, unless explicitly stated otherwise, response time is typically the total time required to reach the steady state (settling time), not just the time to begin responding.

② Time Constant: | Dynamic Characteristics

- Time it takes for the system's response to reach 63.2% of its final value after a step input

③ Bandwidth: | Dynamic Characteristics

- Frequency range over which the system accurately responds

Dynamic Performance Parameters

④ Frequency Response: | Dynamic Characteristics

- It describes how the system behaves when subjected to sinusoidal inputs of varying frequencies.

Amplitude Ratio (Gain)

- The ratio of the output signal amplitude to the input signal amplitude as a function of frequency.

Phase Shift

- The delay (in degrees or radians) between the input and output signals.

Dynamic Performance Parameters

⑤ Rise Time: | Dynamic Characteristics

- Time taken to rise from 10% to 90% of the final value
- Short rise time means a faster system response to inputs.

⑥ Delay Time: | Dynamic Characteristics

- Time between the application of input and the beginning of the output response
- Delays can lead to instability or lag in feedback systems.


Error in Measurement

Error in Measurement

- it is the deviation of the measured value (M.V) from the true value (T.V) of the quantity under measurement.
- so error estimate:

$$\text{error} = \frac{\text{true value} - \text{measured value}}{\text{true value}} \times 100\%$$

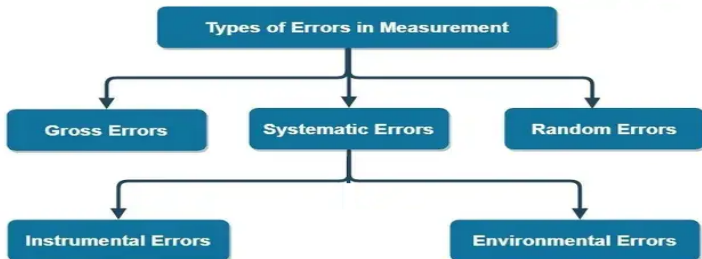- Errors may come from different sources and usually classified to be three main types



Error in Measurement

Gross Error: | Error in Measurement

✓ is the error due to users:

- error in calculation,
- error in observation,
- error in connections,
- error in placement

Corrective Methods:

Careful measurement

At least three measurement for the same quantity by different users.

Error in Measurement

Systematic Error: | Error in Measurement

① **Instrumental Error:**

errors are due to
short-coming of instruments,
less accuracy in scale calibration
errors due to defective parts
improper tension in spring.

Corrective Methods:

use of standard instrument
re-calibration or correct scaling
use of correlation factors

Error in Measurement

Systematic Error: | Error in Measurement

② **Environmental Error:**

variation in temperature, humidity

error due to external electro-static/magnetic field.

Corrective Methods:

measurement in air-conditioned room

compensation for pressure and humidity effect

use of shielding

Error in Measurement

Random Error: | Error in Measurement

- ✓ cause of error is unknown
this type of error can't be corrected

Corrective Methods:

- use of statistical analysis – mean (arithmetic)
- use the statistical analysis only after minimizing gross error and systematic error

Error in Measurement

Random Error: | Error in Measurement

✓ **Statistical Analysis:**

arithmetic mean

deviation

average deviation (\sim zero)

standard deviation / RMS (σ)

variance (v)

Error in Measurement

Summary of Error: | Error in Measurement

Error Type	Crucial When	Why Critical
Gross	Due to human mistakes or negligence	Often large errors; easily preventable
Systematic	When left undetected in long-term measurements or automated systems	Leads to consistently wrong decisions
Random	In ultra-precise systems (e.g., quantum sensors, nanotech)	Affects resolution; can be minimized but not avoided

Errors in Measurement

What is next?

Explore more on:

- ✓ What are the different methods to measure low resistance? see detailed circuit diagram on ammeter-voltmeter method.
- ✓ What is AC/DC bridge? detailed of circuit diagram and mathematics.
- ✓ block diagram and basic relations of arm parameters.
 - ① Wheat-stone bridge,
 - ② maxwell's bridge,
 - ③ Schering's bridge

Measurement of Resistance

Low Resistance Measurement

- there are three types of methods to measure low resistance
 - ① Ammeter - Voltmeter method
 - ② Kelvin's double bridge method
 - ③ Potentio-meter method

Measurement of Resistance

Ammeter-Voltmeter method: | Low Resistance Measurement

- Consider the following circuit diagram:
- measure of Resistance

$$R_m = \frac{V}{I} \quad \rightarrow \quad R = R_m \left[1 + \frac{R_m}{R_v} \right]$$

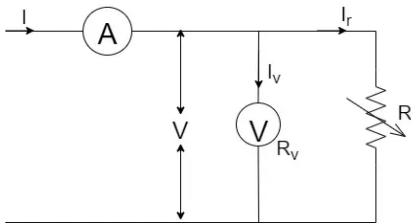


Fig. 1 Measurement of resistance by ammeter-voltmeter method

Measurement of Resistance

Ammeter-Voltmeter method: | Low Resistance Measurement

- Consider the following circuit diagram:

measure of Resistance

$$\begin{aligned} R_m &= \frac{V}{I} \\ &= \frac{V}{I_r + I_v} \\ &= \frac{V}{\frac{V}{R} + \frac{V}{R_v}} \\ &= \frac{R}{1 + \frac{R}{R_v}} \end{aligned}$$

True of Resistance

$$\begin{aligned} R &= \frac{V}{I_r} \\ &= \frac{V}{I - I_v} = \frac{V}{I - \frac{V}{R_v}} \\ &= \frac{V}{I \left(1 - \frac{V}{R_v \times I} \right)} \\ R &= \frac{R_m}{1 - \frac{R_m}{R_v}} \end{aligned}$$

Measurement of Resistance

Wheatstone Bridge – DC Bridge

- A very important circuit used to measure **medium resistance**.

For balanced circuit,
galvanometer current is zero


$$I_1 R_1 = I_2 R_2 \dots\dots(a)$$

$$I_1 = I_3 = \frac{E}{R_1 + R_3} \dots\dots(b)$$

$$I_2 = I_4 = \frac{E}{R_2 + R_4} \dots\dots(c)$$

Substituting I_1 and I_2 from b and c to a
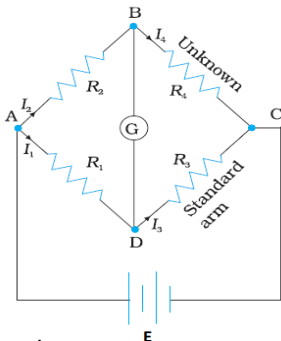
$$R_1 R_4 = R_2 R_3 \rightarrow R_4 = \frac{R_2 R_3}{R_1}$$



Measurement of Impedance Components

AC Bridge

- when excitation voltage or current to the bridge circuit is alternating, the bridge is ac bridge;
- the ac bridge circuit is used to measure impedance components such as inductance, capacitance, loss factor.

✓ For balanced circuit,
current through Detector is zero


$$I_1 Z_1 = I_2 Z_2 \dots\dots(i)$$

$$I_1 = I_3 = \frac{E}{Z_1 + Z_3} \dots\dots(ii)$$

$$I_2 = I_4 = \frac{E}{Z_2 + Z_4} \dots\dots(iii)$$

Substituting I_1 and I_2 from (ii) and (iii) to (i)

$$Z_1 Z_4 = Z_2 Z_3$$

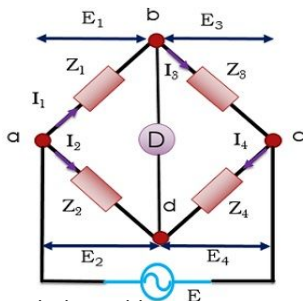


Measurement of Impedance Components

AC Bridge

- ✓ When considered polar form of the impedance;
 - ① the product of magnitude of any two opposite arms impedance must be equal to the product of magnitude of other two arm's impedance.
 - ② the sum of phase angle of any two opposite arm impedance must be equal to that of other two.

- ✓ For balanced circuit, current through Detector is zero
 $Z_1 Z_4 = Z_2 Z_3 \dots (iv)$

$$|Z_1||Z_4|\angle(\theta_1 + \theta_4) = |Z_2||Z_3|\angle(\theta_2 + \theta_3)$$

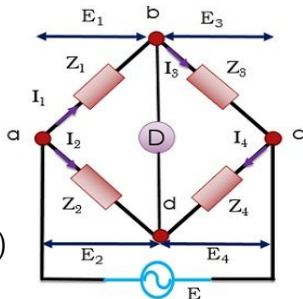

Measurement of Impedance Components

Maxwell's Bridge – AC Bridge

- Inductance L_x is measured in terms of capacitance known.

From the circuit diagram:


$$Z_2 = R_2 \angle 0$$

$$Z_x = R_x + jX_L$$

$$Z_x = R_x + j\omega L_x$$

$$Z_3 = R_3 \angle 0$$

$$Y_1 = \frac{1}{R_1} + j\omega C_1$$

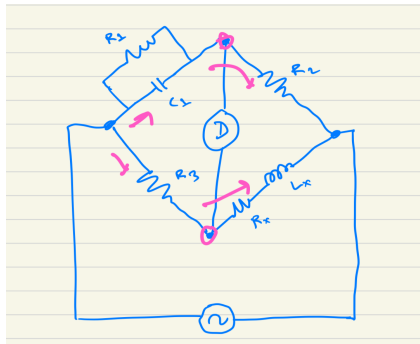

Measurement of Impedance Components

Maxwell's Bridge – AC Bridge

- Inductance L_x is measured in terms of capacitance known.

For balanced AC bridge:

$$Z_1 Z_x = Z_2 Z_3$$

$$Z_x = \frac{Z_2 Z_3}{Z_1} \quad \left(Y_1 = \frac{1}{Z_1} \right)$$


$$Z_x = R_2 R_3 \left(\frac{1}{R_1} + j\omega C_1 \right)$$

$$R_x + j\omega L_x = R_2 R_3 \left(\frac{1}{R_1} + j\omega C_1 \right)$$

$$R_x + j\omega L_x = \frac{R_2}{R_1} R_3 + j\omega R_2 R_3 C_1$$

→ Equating real and imaginary parts:
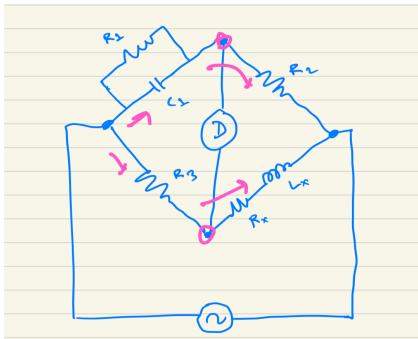
$$R_x = \frac{R_2}{R_1} R_3 \dots\dots (i) \quad L_x = R_2 R_3 C_1 \dots\dots (ii)$$



Measurement of Impedance Components

Schering's Bridge – AC Bridge


- A very important circuit used to measure **Capacitance**.

$$Y_1 = \frac{1}{R_1} + j\omega C_1$$

$$Z_2 = R_2$$

$$Z_x = R_x - j\frac{1}{\omega C_x}$$

$$Z_3 = -j\frac{1}{\omega C_3}$$

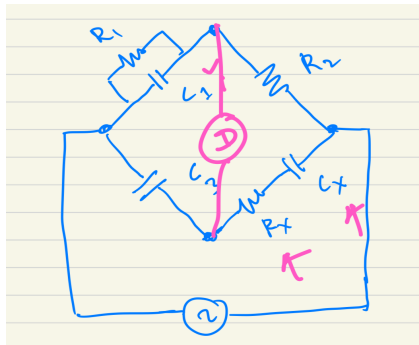

Measurement of Impedance Components

Schering's Bridge – AC Bridge

- A very important circuit used to measure **Capacitance**.

For balanced circuit,

Detector current is zero

$$Z_1 Z_x = Z_2 Z_3$$


$$Z_x = Z_2 Z_3 Y_1$$

$$R_x - j \frac{1}{\omega C_x} = R_2 \left(-\frac{j}{\omega C_3} \right) \left(\frac{1}{R_1} + j \omega C_1 \right)$$

$$R_x - j \frac{1}{\omega C_x} = -j \frac{R_2}{\omega R_1 C_3} + R_2 \frac{C_1}{C_3}$$

→ Equating real and imaginary parts:
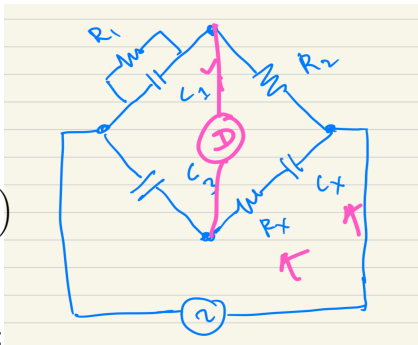
$$R_x = \frac{C_1}{C_3} R_2 \dots \dots (i) \quad C_x = \frac{R_1}{R_2} C_3 \dots \dots (ii)$$



Maxwell's and Schering's Bridge

Comparative block Diagram

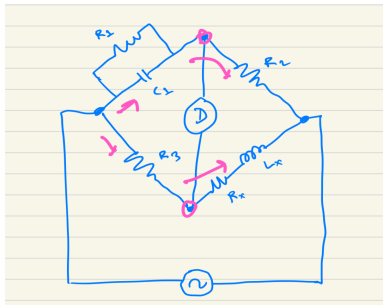


Fig. 2 Maxwell's Bridge

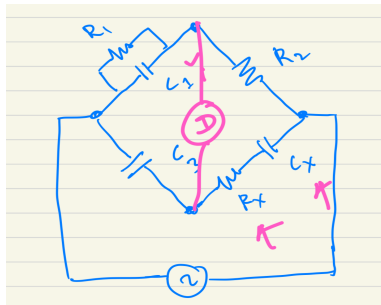


Fig. 3 Schering's Bridge

As you go Assignment

Assignment Module#2 is available at MS-Team.

Submission Deadline: 30th May 2025 (*Before 3:00 PM*)